

# CE653 – Asynchronous Circuit Design

Instructor: C. Sotiriou

<http://inf-server.inf.uth.gr/courses/CE653/>

1

CE-653 - Hazards and Analysis Methods 18/3/2014

## Contents

---


- ▶ Eichelberger's paper examples
- ▶ Abramovic's Book
- ▶ Methods for Hazard/Race Detection
  - ▶ Combinational Circuits
  - ▶ Sequential Circuits

---

▶ 2

CE-653 - Hazards and Analysis Methods 18/3/2014

## Motivation - C-Element Hazard Example

 

### ► Consider:



1.  $(a, b) = 11 \rightarrow ab = 1 \rightarrow c = 1$  (before  $ac, bc = 1$ )
2.  $(a, b) = 10 \rightarrow ab = 0 \rightarrow c = 0, ac = 1 \rightarrow c = 1$  (static 1 hazard)

► 3

CE-653 - Hazards and Analysis Methods 18/3/2014

## Motivation - C-Element Hazard Example

### ► Hazard Animation:

  

► 4

CE-653 - Hazards and Analysis Methods 18/3/2014

## Asynchronous Circuits - Classes

### ► Dimension 1: Delay Model

- Measure of robustness of control to variations in delays of gates and wires
- Assumption about delays of gates necessary to ensure design works as dictated by specification
  - Most robust = Arbitrary gate and wire delay
    - Design will work as specified even if delays are random(0,infinity)
    - Larger delays just means control is slower
  - Least robust = Bounded delay on gates and wires
    - If delays are outside these bounds, glitches may occur at outputs or output simply may not transition as expected

### ► Dimension 2: Environmental Model

- Essentially these are assumptions/restrictions on how fast environment can be for circuit to work


► 5

CE-653 - Hazards and Analysis Methods 18/3/2014

## QDI Model – Isochronic Fork
 
### ► Isochronic fork

- If fork at F is isochronic
  - can assume B fires high before A
  - translates to relative timing assumption about long and short paths



► 6

CE-653 - Hazards and Analysis Methods 18/3/2014

## Asynchronous Circuits - Classes


- ▶ Timing Model (or Class) is used to define specific timing assumptions with respect to correct circuit operation
  - ▶ DI
    - ▶ Arbitrary gate and wire delays (unbounded)
  - ▶ QDI
    - ▶ DI except for Isochronic Forks
      - No need to acknowledge fanouts
  - ▶ SI (or Muller) circuits
    - ▶ Arbitrary gate delays, bounded wire delays
    - ▶ Closed system implementation (gate + environment)
  - ▶ Fundamental Mode (Huffman) circuits
    - ▶ “Fundamental Mode” Operation:
      - ▶ **Outputs and State (local) stabilise before new input change**

▶ 7

CE-653 - Hazards and Analysis Methods 18/3/2014
 
## Hazard Types

- ▶ Static 0 or 1
- ▶ Function Hazard
  - ▶  $f(A) = f(B)$ , where:
    - ▶  $A = (a_1, \dots, a_p, a_{p+1}, \dots, a_n)$
    - ▶  $B = (\underline{a_1'}, \dots, \underline{a_p'}, a_{p+1}, \dots, a_n)$
    - ▶  $A \rightarrow B$  input vector transition contains 0's and 1's in function cubes
- ▶ Logic Hazard
  - ▶ Combinational Network
    - static hazard caused by gate delays
- ▶ Dynamic
  - ▶ Static + Output Change



▶ 8

CE-653 - Hazards and Analysis Methods 18/3/2014

## Function Hazard Example

- Consider input transitions:  
000 → 110 for function f

		x, y			
		00	01	11	10
z	0	1 <sup>a</sup>	0 <sup>b</sup>	1 <sup>c</sup>	1 <sup>d</sup>
	1	1	0	0	0

f


- Function f contains potential function hazards:
  - for input changes between minterms  
a → c, a → d, etc. – static 1
  - for input changes between other minterms,  
e.g. 010 → 111 – static 0

9

CE-653 - Hazards and Analysis Methods 18/3/2014
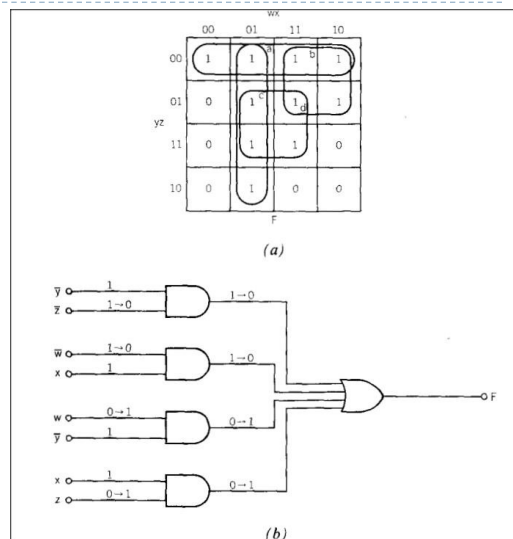
## Logic Network Example

- Logic Networks may be free of function hazards but not of logic hazards
- Consider transitions between minterms:
  - a → d, d → a, c → b, b → c
- Theorem:**  
A 2-level SOP function f is free of logic hazards, iff it contains all Primes (PIs) of f.




10

CE-653 - Hazards and Analysis Methods 18/3/2014
 
## Ternary Approximation to Binary Signals

- ▶ A third value,  $1/2$ , or **X**, may be used to signify the transitive state of a signal
- ▶ 3-Valued Algebra may be used to detect and eliminate hazards



▶ 11

CE-653 - Hazards and Analysis Methods 18/3/2014

## Binary and Ternary XOR gate Truth Table

		x	
		0	1
y	0	0 <sup>a</sup>	1 <sup>b</sup>
	1	1 <sup>c</sup>	0 <sup>d</sup>

**G**

		x		
		0	$\frac{1}{2}$	1
y	0	0 <sup>i</sup>	$\frac{1}{2}$ <sup>j</sup>	1
	$\frac{1}{2}$	$\frac{1}{2}$	$\frac{1}{2}$ <sup>k</sup>	$\frac{1}{2}$
	1	1	$\frac{1}{2}$	0

**G\***

- ▶ Original truth table of logic function used to determine ternary truth table, whereas  $\frac{1}{2} = \mathbf{0 \text{ OR } 1}$ , e.g. for XOR:
  - ▶  $0 (+) \frac{1}{2} = 0 (+) (0 \text{ or } 1) = 1/2$ , as  $0 (+) 0$  and  $0 (+) 1$  produce different outputs
  - ▶  $\frac{1}{2} (+) \frac{1}{2} = (0 \text{ or } 1) (+) (0 \text{ or } 1) = \frac{1}{2}$
- ▶ if p of n inputs are  $\frac{1}{2}$ , output is 0 or 1 if all  $2^p$  output entries agree

▶ 12

CE-653 - Hazards and Analysis Methods 18/3/2014

## Ternary Truth tables for AND/OR

		x		
		0	$\frac{1}{2}$	1
y	0	0	0	0
	$\frac{1}{2}$	0	$\frac{1}{2}$	$\frac{1}{2}$
	1	0	$\frac{1}{2}$	1

AND  
 $G^* = \text{MIN}(x, y)$

		x		
		0	$\frac{1}{2}$	1
y	0	0	$\frac{1}{2}$	1
	$\frac{1}{2}$	$\frac{1}{2}$	$\frac{1}{2}$	1
	1	1	1	1

OR  
 $G^* = \text{MAX}(x, y)$

- ▶ AND, OR truth tables easier to derive due to their controlling values:
  - ▶  $0 \cdot \frac{1}{2} = 0, 1 + \frac{1}{2} = 1$

▶ 13

CE-653 - Hazards and Analysis Methods 18/3/2014

## Ternary Gate Functions Properties

- ▶ Property 1:
  - ▶ If one or more ternary gate or logic network inputs are changed  $1 \rightarrow \frac{1}{2}$ , or  $0 \rightarrow \frac{1}{2}$ , the ternary outputs will either remain unchanged or change to  $\frac{1}{2}$
- ▶ Property 2:
  - ▶ If one or more ternary gate or logic network inputs are changed  $\frac{1}{2} \rightarrow 1$ , or  $\frac{1}{2} \rightarrow 0$ , the ternary outputs will either remain unchanged or change to 0 or 1
- ▶ Proof:
  - ▶ E.B. Eichelberger – *Hazard Detection in Combinational and Sequential Switching Circuits*, IBM Journal, 1965.

▶ 14

CE-653 - Hazards and Analysis Methods 18/3/2014

## Hazard Detection using Ternary Algebra

### ► Theorem 1:

- A combinational logic network contains a hazard for an input vector transition from A to B, where:

- $A = (a_1, \dots, a_p, a_{p+1}, \dots, a_n)$

- $B = (\underline{a_1}, \dots, \underline{a_v}, a_{p+1}, \dots, a_n)$

- $A/B = (\underline{1/2}, \dots, \underline{1/2}, a_{p+1}, \dots, a_n)$

- iff (if and only if)

1.  $f(A) = f(B) \neq 1/2$

2.  $f(A/B) = 1/2$

### ► Proof:

- Based on previous properties

► 15

CE-653 - Hazards and Analysis Methods 18/3/2014

## Hazard Detection using Ternary Algebra

- For functions  $f_1, f_2$

- Consider input change:

- $w'x'y' \rightarrow wx'y'$

- is a hazard produced for  $f_1, f_2$ ?


- Must determine:

- $f(w', x', y')$ ,
  - $f(\underline{1/2}, \underline{1/2}, y')$ ,
  - $f(w, x, y')$

- Outcome:

- $(1, \underline{1/2}, 1)$

- $f_1, f_2$  both contain a hazard

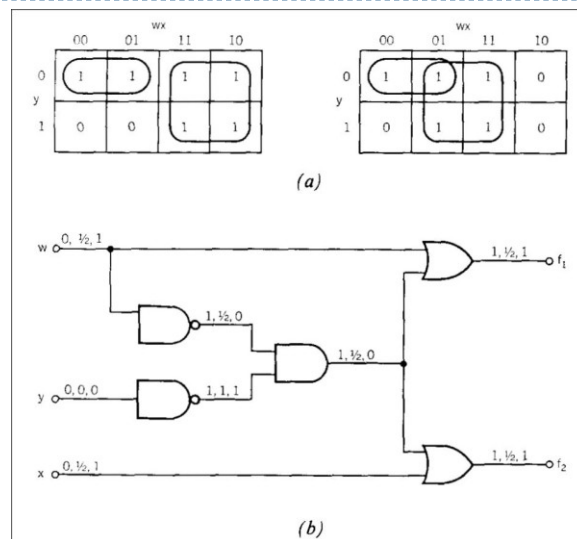

► 16

CE-653 - Hazards and Analysis Methods 18/3/2014



## Additional Hazards in Sequential Circuits

- ▶ **Critical Race**
  - ▶ If order of changes in state variables affects final state, race is critical
  - ▶  $11 \rightarrow 10 \rightarrow 00$ , or,  $11 \rightarrow 01 \rightarrow 00$
- ▶ **Essential Hazard**
  - ▶ Critical race between input and feedback change – must add delay to fix
  - ▶ Property of FSM specification
- ▶ **Essential Hazard Detection:**
  - ▶ for input vector  $A \rightarrow B$ ,
  - ▶ If single change (A, B) produces different states and output to three change times (A  $\rightarrow$  B, A, B) circuit contains an **Essential Hazard**


▶ 17

CE-653 - Hazards and Analysis Methods 18/3/2014

## Essential Hazard Example

	x	
y1y0	0	1
1 (00)	1, 0	2, 0
2 (01)	3, 0	2, 0
3 (11)	3, 0	4, 0
4 (10)	1, 1	4, 1

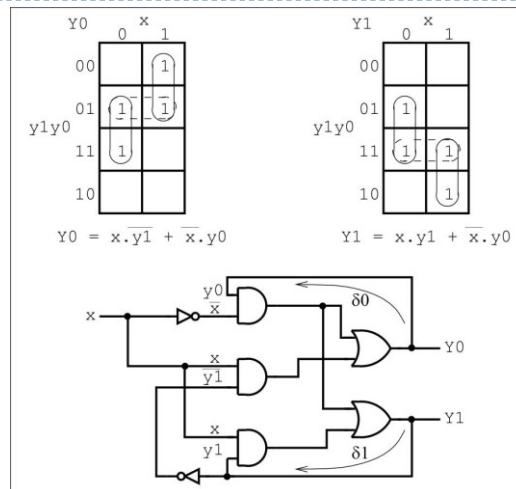
- ▶  $\delta_0, \delta_1$  are feedback delays for state signals  $Y1, Y0$ 
  - ▶  $Y1, Y0 \rightarrow y1, y0$



▶ 18

CE-653 - Hazards and Analysis Methods 18/3/2014

## Sequential Hazard Analysis

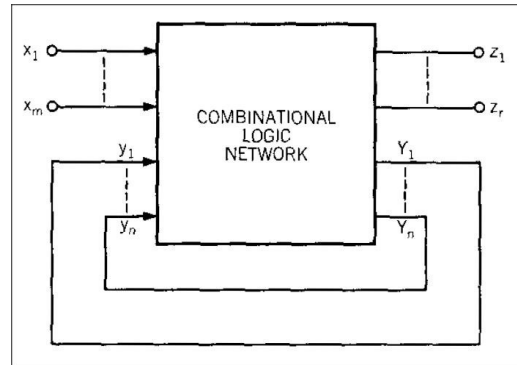

### ▶ Sequential Circuit Model:

- ▶ Input vector ( $x_1 \dots x_m$ ) changes
- ▶ Next State signals ( $Y_1 \dots Y_n$ ) change as a response to input change
- ▶ Current State signals ( $y_1 \dots y_n$ ) change as a response to next state change

▶ 19

CE-653 - Hazards and Analysis Methods 18/3/2014

## Sequential Hazard Analysis

### ▶ Eichelberger's Two-Step Approach:

#### ▶ Procedure/Step 1 – Determine all **changing** $Y$ signals

1. Set changing input vector signals to intermediate  $1/2$  values, and all other  $x$  or  $y$  signals to their previous values
2. Evaluate  $Y_i$  functions to determine changes from 1 or 0 to  $1/2$
3. Propagate any  $1/2 Y_i$  change to corresponding  $y_i$  change and repeat process until no further changes to  $Y_i$  occur

#### ▶ Procedure/Step 2 – Determine all **stabilising** $Y$ signals

- ▶ Set changing input vector signals to their final values, 1 or 0, and all other  $x$  or  $y$  signals to their previous values, as determined by Procedure 1
- ▶ Evaluate  $Y_i$  functions to determine changes from  $1/2$  to 1 or 0
- ▶ Propagate any 0 or 1  $Y_i$  change to corresponding  $y_i$  change and repeat process until no further changes to  $Y_i$  occur

▶ 20

CE-653 - Hazards and Analysis Methods 18/3/2014

## Sequential Hazard Analysis

### ► Theorem 2:

- If  $Y_k = 1(0)$  after applying Procedures A and B to a sequential circuit for a given input change starting from a given internal state, then the  $Y_k$  signal must stabilise at 1(0) for this transition, regardless of the values of the finite delays of the logic gates

### ► Proof:


- Based on previous Theorem (Theorem 1)

► 21

CE-653 - Hazards and Analysis Methods 18/3/2014
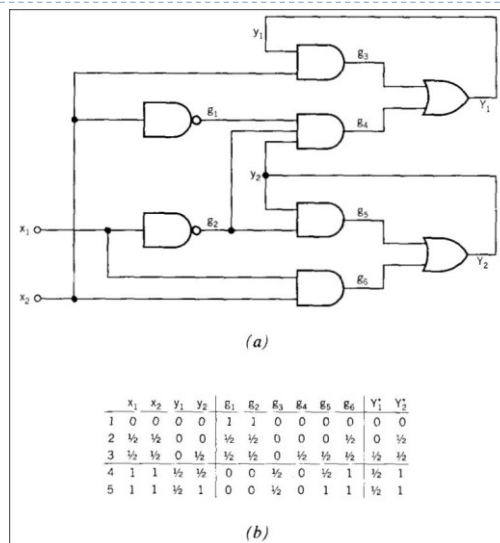
## Sequential Hazard Analysis - Example

- Determine whether  $00 \rightarrow 11$  change in  $x_1, x_2$  inputs results in indeterminate final state



► 22

CE-653 - Hazards and Analysis Methods 18/3/2014

## Ternary Simulation Characteristics

- ▶ For  $n$  feedback lines, at most  $2 \times n$  evaluations are required
- ▶ Hazards and Races are detected automatically
- ▶ **Optimisations**
  - ▶ During Procedure A, any gate with output at 1/2 need not be further considered, since output cannot change further
  - ▶ During Procedure B, any gate with output different from 1/2 need not be further considered, since again its output cannot change further
    - ▶ In both cases remove gate from simulation queue

## From Ternary to 13-Value Logic for Hazard Detection

## 13-Value Logic

### ► Goal:

- Separate hazards (1/2 value is X here) from transitions
- Previous algorithms are often very pessimistic for many types of asynchronous circuits
- Each triplet represents transition from a signal state to another and the intermediate state, e.g.  $\langle 1, \vee, 0 \rangle$

**Constant:**  $\langle 1, 1, 1 \rangle, \langle 0, 0, 0 \rangle$

**Transition:**  $\langle 0, \uparrow, 1 \rangle, \langle 1, \downarrow, 0 \rangle$

**Hazard:**  $\langle 0, X, 0 \rangle, \langle 0, X, 1 \rangle, \langle 1, X, 0 \rangle, \langle 1, X, 1 \rangle$

**Stabilizing:**  $\langle X, X, 0 \rangle, \langle X, X, 1 \rangle$

**Destabilizing:**  $\langle 0, X, X \rangle, \langle 1, X, X \rangle$

**Undefined:**  $\langle X, X, X \rangle$

► 25

CE-653 - Hazards and Analysis Methods 18/3/2014


## 13-Value AND Gate Truth Table

	$\langle 0, X, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, X \rangle$	$\langle 1, X, 0 \rangle$	$\langle 1, X, 1 \rangle$	$\langle 1, X, X \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 1 \rangle$	$\langle X, X, X \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, \wedge, 1 \rangle$	$\langle 1, 1, 1 \rangle$	$\langle 1, \vee, 0 \rangle$
$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$
$\langle 0, X, 1 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, 0 \rangle$
$\langle 0, X, X \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, X \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, 0 \rangle$
$\langle 1, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 1, X, 0 \rangle$	$\langle 1, X, 0 \rangle$	$\langle 1, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 1, X, 0 \rangle$	$\langle 1, X, 0 \rangle$
$\langle 1, X, 1 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, X \rangle$	$\langle 1, X, 0 \rangle$	$\langle 1, X, 1 \rangle$	$\langle 1, X, X \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 1 \rangle$	$\langle X, X, X \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 1, X, 1 \rangle$	$\langle 1, X, 0 \rangle$
$\langle 1, X, X \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, X \rangle$	$\langle 1, X, 0 \rangle$	$\langle 1, X, X \rangle$	$\langle 1, X, X \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 1 \rangle$	$\langle X, X, X \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, X, X \rangle$	$\langle 1, X, X \rangle$	$\langle 1, X, 0 \rangle$
$\langle X, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 0 \rangle$
$\langle X, X, 1 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, X \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 1 \rangle$	$\langle X, X, X \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 1 \rangle$	$\langle X, X, X \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle X, X, 1 \rangle$	$\langle X, X, 0 \rangle$
$\langle X, X, X \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, X \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, X \rangle$	$\langle X, X, X \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, X \rangle$	$\langle X, X, X \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, X, X \rangle$	$\langle X, X, X \rangle$	$\langle X, X, 0 \rangle$
$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, 0, 0 \rangle$
$\langle 0, \wedge, 1 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, X \rangle$	$\langle 0, 0, 0 \rangle$	$\langle \wedge, 1 \rangle$	$\langle 0, \wedge, 1 \rangle$	$\langle 0, \vee, 0 \rangle$
$\langle 1, 1, 1 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 1 \rangle$	$\langle 0, X, X \rangle$	$\langle 1, X, 0 \rangle$	$\langle 1, X, 1 \rangle$	$\langle 1, X, X \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 1 \rangle$	$\langle X, X, X \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, \wedge, 1 \rangle$	$\langle 1, 1, 1 \rangle$	$\langle 1, \vee, 0 \rangle$
$\langle 1, \vee, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 1, X, 0 \rangle$	$\langle 1, X, 0 \rangle$	$\langle 1, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle X, X, 0 \rangle$	$\langle 0, 0, 0 \rangle$	$\langle 0, X, 0 \rangle$	$\langle 1, \vee, 0 \rangle$	$\langle 1, \vee, 0 \rangle$

► 26

CE-653 - Hazards and Analysis Methods 18/3/2014

## 13-Value Example

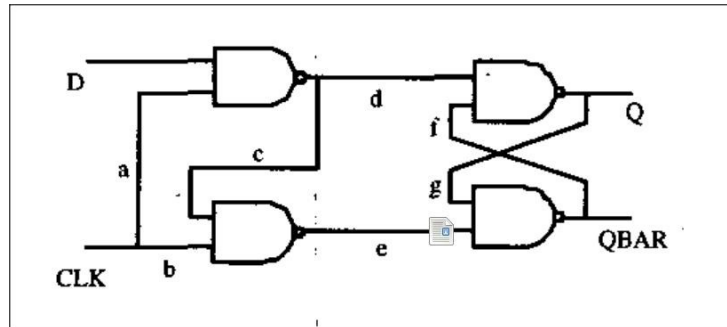

- ▶ CLK =  $\langle 1, v, 0 \rangle$ , D =  $\langle 1, 1, 1 \rangle$
- ▶ Evaluate node e
  - ▶  $a = b = \langle 1, v, 0 \rangle$ ,  $c = \langle 0, ^, 1 \rangle$ ,  $e = \langle 1, X, 1 \rangle$
- ▶ Very conservative as it is based on zero delay gate model
  - ▶ assumes no control over gate delays

▶ 27

CE-653 - Hazards and Analysis Methods 18/3/2014


## Timestamps – Preserving Relative Transition Order

- ▶ maintaining the relative order of transitions, based on finite gate delays, can be achieved via **timestamps**
- ▶ **Timestamp** is a pair (i, t)
  - ▶ i – signal group id – used to indicate causal transitions
  - ▶ t – time field – always increments
- ▶ Timestamps are only kept for signal transitions:
  - $\langle 0, ^, 1 \rangle$ ,  $\langle 1, v, 0 \rangle$  - not necessary for other values
- ▶ Generating the i field for a multi-input gate (AND, OR)
  - ▶ If output result stems from input changes of same group (while other inputs remain stable)  $\rightarrow$  *group id remains the same*
  - ▶ Else if output result stems from input changes of multiple groups  $\rightarrow$  *generate new group id for the output signal and mark as successor*
- ▶ Successor group ids indicated via *group mask* of signal
  - ▶ bit per predecessor of current group id – 1 indicates true, 0 false

▶ 28

CE-653 - Hazards and Analysis Methods 18/3/2014

## Gate Evaluation with Timestamps

 


- ▶ When inputs have same group id, they imply a relative order
  - ▶ Thus their evaluation is not performed via truth-table, but unfolds time into multiple phases
- ▶ Example above:
  - ▶ First time frame – inputs  $\langle 1, \vee, 0 \rangle, \langle 0, 0, 0 \rangle$
  - ▶ Second time frame – inputs  $\langle 0, 0, 0 \rangle, \langle 0, \wedge, 1 \rangle$
  - ▶ No hazard at output

▶ 29

CE-653 - Hazards and Analysis Methods 18/3/2014
 
## Timestamps Example

- ▶ In this example both inputs come from different groups:  $i1, i2$ 
  - ▶ Thus a new group id,  $i3$ , is generated



- ▶ cases (a), (b): output transition depends on both input transitions
- ▶ cases (c), (d): output transition depends on first input transition
- ▶ Cases (a), (b):  $i3$  is denoted as successor of  $i1, i2$ 
  - ▶ Group masks:
    - ▶  $i1i2i3(i1) = 100, i1i2i3(i2) = 010, i3i2i1(i3) = 011$
- ▶ Cases (c), (d):  $i3$  is not denoted as successor of  $i1, i2$

▶ 30

CE-653 - Hazards and Analysis Methods 18/3/2014


## 13-Value coupled with Timing

### ► At fanout points:

- Different gate delays → different group ids for same input transition at fanout
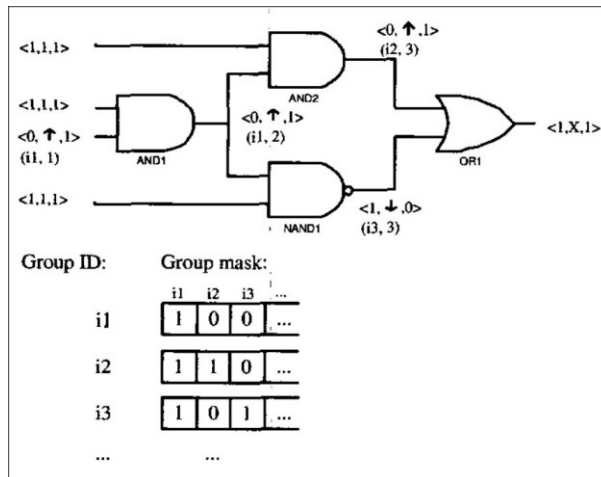
### ► In RHS example:

- Relative order between outputs of NAND, AND not guaranteed
- Outputs assigned new group ids  $i_2$ ,  $i_3$
- Timing is incremented by 1
- Not necessarily by actual gate delay



► 31

CE-653 - Hazards and Analysis Methods 18/3/2014

## Sequential Hazard Analysis

### ► Can be extended with 13-value logic and timeframes:

#### ► Eichelberger's Two-Step Approach:


- Procedure/Step 1 – Determine all **changing**  $Y$  signals
  1. Set changing input vector signals to intermediate  $1/2$  values, and all other  $x$  or  $y$  signals to their previous values
  2. Evaluate  $Y_i$  functions to determine changes from 1 or 0 to  $1/2$
  3. Propagate any  $1/2 Y_i$  change to corresponding  $y_i$  change and repeat process until no further changes to  $Y_i$  occur
- Procedure/Step 2 – Determine all **stabilising**  $Y$  signals
  - Set changing input vector signals to their final values, 1 or 0, and all other  $x$  or  $y$  signals to their previous values, as determined by Procedure 1
  - Evaluate  $Y_i$  functions to determine changes from  $1/2$  to 1 or 0
  - Propagate any 0 or 1  $Y_i$  change to corresponding  $y_i$  change and repeat process until no further changes to  $Y_i$  occur

► 32

CE-653 - Hazards and Analysis Methods 18/3/2014



## C-Element Hazard Example

 

- ▶ How do we analyse this circuit?
  - ▶ Ternary Sequential Hazard Analysis Approach?
  - ▶ 13-value Logic Approach?
  - ▶ Differences?

▶ 33

CE-653 - Hazards and Analysis Methods 18/3/2014

## C-Element Hazard Example

- ▶ Ternary Analysis for  $00 \rightarrow 11 \rightarrow 10$  transitions

Time Frame	a	b	ab	bc	ac	C	c
1	0	0	0	0	0	0	0
2	1/2	1/2	1/2	0	0	1/2	0
3	1/2	1/2	1/2	0	0	1/2	1/2
4	1/2	1/2	1/2	1/2	1/2	1/2	1/2
5	1	1	1	1/2	1/2	1	1/2
6	1	1	1	1/2	1/2	1	1
7	1	1	1	1	1	1	1
8	1	1/2	1/2	1/2	1	1	1
9	1	0	0	0	1	1	1

- ▶ Does not detect sequential hazard – why?
  - ▶ No assumption in timing between  $11 \rightarrow 10$  transitions (Fundamental Mode Operation)

▶ 34

CE-653 - Hazards and Analysis Methods 18/3/2014

## C-Element Hazard Example

- ▶ 13-value Logic equivalent for  $00 \rightarrow 11 \rightarrow 01$  transitions

Time Frame	a	b	ab	ba	ac	C	c
1	<0, 0, 0>	<0, 0, 0>	<0, 0, 0>	<0, 0, 0>	<0, 0, 0>	<0, 0, 0>	<0, 0, 0>
2	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, 0, 0>	<0, 0, 0>	<0, ^, 1>	<0, 0, 0>
3	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, 0, 0>	<0, 0, 0>	<0, ^, 1>	<0, ^, 1>
4	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>
5	<1, v, 0>	<0, ^, 1>	<0, X, 1>	<0, ^, 1>	<0, ^, 1>	<0, X, 1>	<0, ^, 1>
6	<1, v, 0>	<0, ^, 1>	<0, X, 1>	<0, X, 1>	<0, X, 1>	<0, X, 1>	<0, X, 1>

Circuit has not settled!

- ▶ By not letting **inputs** settle, 13-value logic detects hazard!

▶ 35

CE-653 - Hazards and Analysis Methods 18/3/2014

## C-Element Hazard Example - 2

- ▶ 13-value Logic equivalent for  $00 \rightarrow 11 \rightarrow 10$  transitions

Time Frame	a	b	ab	ba	ac	C	c
1	<0, 0, 0>	<0, 0, 0>	<0, 0, 0>	<0, 0, 0>	<0, 0, 0>	<0, 0, 0>	<0, 0, 0>
2	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, 0, 0>	<0, 0, 0>	<0, ^, 1>	<0, 0, 0>
3	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, 0, 0>	<0, 0, 0>	<0, ^, 1>	<0, ^, 1>
4	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>	<0, ^, 1>
5	<1, 1, 1>	<1, v, 0>	<1, v, 1>	<1, ^, 1>	<0, ^, 1>	<1, X, 1>	<0, ^, 1>
6	<1, 1, 1>	<1, v, 0>	<1, v, 1>	<1, ^, 1>	<0, ^, 1>	<1, X, 1>	<1, X, 1>

- ▶ By not letting **feedback** settle, 13-value logic detects hazard!

▶ 36

CE-653 - Hazards and Analysis Methods 18/3/2014

## Another Approach to Hazards – Semi-modular Analysis

37

CE-653 - Hazards and Analysis Methods 18/3/2014

## Semi-Modularity and Computation Interference

- ▶ Semi-modularity is a key property for designing hazard-free asynchronous systems
- ▶ Definition [*Semi-Modularity*]
  - ▶ a circuit is *semi-modular*, iff an output transition which has been enabled to fire (by an input transition) CANNOT subsequently be disabled (by a subsequent input transition)
- ▶ Semi-modularity forces output acknowledgement
  - ▶ Input → Output → next Input → ...
  - ▶ Thus leading to hazard-free SI systems
- ▶ Computation Interference
  - ▶ Violation of Semi-modularity
  - ▶ Example: AND2 gate with I I inputs should present  $\wedge$  rise transition before  $\vee$  in inputs

▶ 38

CE-653 - Hazards and Analysis Methods 18/3/2014

## Semi-Modular FSM Specifications of Combinational Gates

Total State a b out (a.b)	00	01	10	11
000	000	010	100	110
001	000	X	X	X
010	X	010	X	110
011	X	010	X	110
100	X	X	100	110
101	X	X	100	X
110	X	X	X	111
111	001	011	101	111

- ▶ Arrows: states where the gate output will fire
- ▶ Not accepting new inputs