

CAD Algorithms for Physical Design -
Netlist Hierarchy and Connectivity
Representation

Christos P Sotiriou

Contents

- ▶ Verilog Hierarchy
- ▶ Alternative Representations
 - ▶ Gatepin-level Connectivity (Direct)
 - ▶ Net-based Connectivity (Indirect)

Wire = Net = input/output

Hierarchical Netlist Example

counter-MAPPED7.v

```
module counter_DW01_inc_0 ( A, SUM );
input [7:0] A;
output [7:0] SUM;
wire [7:2] carry;

adhalf_1 U1_1_6 ( .a(A[6]), .b(carry[6]), .co(carry[7]), .s(SUM[6]) );
adhalf_1 U1_1_1 ( .a(A[1]), .b(A[0]), .co(carry[2]), .s(SUM[1]) );
adhalf_1 U1_1_2 ( .a(A[2]), .b(carry[2]), .co(carry[3]), .s(SUM[2]) );
adhalf_1 U1_1_3 ( .a(A[3]), .b(carry[3]), .co(carry[4]), .s(SUM[3]) );
adhalf_1 U1_1_4 ( .a(A[4]), .b(carry[4]), .co(carry[5]), .s(SUM[4]) );
adhalf_1 U1_1_5 ( .a(A[5]), .b(carry[5]), .co(carry[6]), .s(SUM[5]) );
inv_2 U1 ( .a(A[0]), .x(SUM[0]) );
xor2_1 U2 ( .a(carry[7]), .b(A[7]), .x(SUM[7]) );
endmodule

module counter ( clk, reset, count );
output [7:0] count;
input clk, reset;
wire [7:0] internal;
wire n18;

counter_DW01_inc_0 add_13 ( .A(count), .SUM(internal[7:0]) ); // not multinet - {} //
dffpr_2 \count_reg[7] ( .d(internal[7]), .ck(clk), .rb(n18), .q(count[7]) );
dffpr_2 \count_reg[4] ( .d(internal[4]), .ck(clk), .rb(n18), .q(count[4]) );
dffpr_2 \count_reg[5] ( .d(internal[5]), .ck(clk), .rb(n18), .q(count[5]) );
dffpr_2 \count_reg[6] ( .d(internal[6]), .ck(clk), .rb(n18), .q(count[6]) );
dffpr_2 \count_reg[2] ( .d(internal[2]), .ck(clk), .rb(n18), .q(count[2]) );
dffpr_2 \count_reg[3] ( .d(internal[3]), .ck(clk), .rb(n18), .q(count[3]) );
dffpr_2 \count_reg[1] ( .d(internal[1]), .ck(clk), .rb(n18), .q(count[1]) );
dffpr_2 \count_reg[0] ( .d(internal[0]), .ck(clk), .rb(n18), .q(count[0]) );
inv_2 U4 ( .a(reset), .x(n18) );
endmodule
```


▶ 3

CE439 - CAD Algorithms II 28/7/2017

Gatepin-Level Connectivity Representation


- ▶ No Nets/Wires stored, only gatepin to gatepin connections
 - ▶ Similar to a graph representation where gatepins are nodes
- ▶ Gatepin
 - ▶ Each gatepin is connected to a list of gatepins
 - ▶ Its connected gatepins may be Module I/O gatepins
- ▶ Simple Representation
- ▶ Redundancy
 - ▶ As connections of $a \rightarrow b$ are stored both in a and in b

Partial Schematic

 

Gatepin-based Connectivity

Gatepins:

 


```

Gate Pin: counter_DW01_inc_0/A17
Connections: (4)
counter_DW01_inc_0/U2/b (no delay info)
counter/count7 (no delay info)
counter/add_13/A17 (no delay info)
counter/\count_reg[7]/q (no delay info)
-----
Gate Pin: counter_DW01_inc_0/SUM17
Connections: (3)
counter_DW01_inc_0/U2/x (no delay info)
counter/add_13/SUM17 (no delay info)
counter/\count_reg[7]/d (no delay info)
-----
Gate Pin: counter/\count_reg[7]/d
Connections: (2)
counter/add_13/SUM17 (no delay info)
counter_DW01_inc_0/SUM17 (no delay info)
-----
Gate Pin: counter/count7
Connections: (3)
counter/add_13/A17 (no delay info)
counter_DW01_inc_0/A17 (no delay info)
counter/\count_reg[7]/q (no delay info)
-----
Gate Pin: counter_DW01_inc_0/U1_1_6/co
Connections: (1)
counter_DW01_inc_0/U2/a (no delay info)
-----
Gate Pin: counter/\count_reg[7]/q
Connections: (3)
counter/count7 (no delay info)
counter/add_13/A17 (no delay info)
counter_DW01_inc_0/A17 (no delay info)
    
```

- ▶ **Tracing Gatepin**
counter/count_reg[7]/q connections?
- ▶ **Tracing Gatepin**
counter/count_reg[7]/d connections?

Gatepin-based Connectivity

Gatepins:

 

```

Gate Pin: counter_DW01_inc_0/A17
Connections: (4)
counter_DW01_inc_0/U2/b (no delay info)
counter/count[7] (no delay info)
counter/add_13/A17 (no delay info)
counter/\count_reg[7]/q (no delay info)
-----
Gate Pin: counter_DW01_inc_0/SUM17
Connections: (3)
counter_DW01_inc_0/U2/x (no delay info)
counter/add_13/SUM17 (no delay info)
counter/\count_reg[7]/d (no delay info)
-----
Gate Pin: counter/\count_reg[7]/d
Connections: (2)
counter/add_13/SUM17 (no delay info)
counter_DW01_inc_0/SUM17 (no delay info)
-----
Gate Pin: counter/count[7]
Connections: (3)
counter/add_13/A17 (no delay info)
counter_DW01_inc_0/A17 (no delay info)
counter/\count_reg[7]/q (no delay info)
-----
Gate Pin: counter_DW01_inc_0/U1_1_6/co
Connections: (1)
counter_DW01_inc_0/U2/a (no delay info)
-----
Gate Pin: counter/\count_reg[7]/q
Connections: (3)
counter/count[7] (no delay info)
counter/add_13/A17 (no delay info)
counter_DW01_inc_0/A17 (no delay info)


```

Connected gatepins

- ▶ Tracing Gatepin
counter/count_reg[7]/q connections?
- ▶ Tracing Gatepin
counter/count_reg[7]/d connections?

Gatepin-based Connectivity

Gatepins:

 

```
Gate Pin: counter_DW01_inc_0/A17
Connections: (4)
counter_DW01_inc_0/U2/b (no delay info)
counter/count[7] (no delay info)
counter/add_13/A17 (no delay info)
counter/\count_reg[7]/q (no delay info)
```

Next level
of
Connected
gatepins

```
Gate Pin: counter_DW01_inc_0/SUM17
Connections: (3)
counter_DW01_inc_0/U2/x (no delay info)
counter/add_13/SUM17 (no delay info)
counter/\count_reg[7]/d (no delay info)
```

```
Gate Pin: counter/\count_reg[7]/d
Connections: (2)
counter/add_13/SUM17 (no delay info)
counter_DW01_inc_0/SUM17 (no delay info)
```

```
Gate Pin: counter/count[7]
Connections: (3)
counter/add_13/A17 (no delay info)
counter_DW01_inc_0/A17 (no delay info)
counter/\count_reg[7]/q (no delay info)
```

```
Gate Pin: counter_DW01_inc_0/U1_1_6/co
Connections: (1)
counter_DW01_inc_0/U2/a (no delay info)
```


```
Gate Pin: counter/\count_reg[7]/q
Connections: (3)
counter/count[7] (no delay info)
counter/add_13/A17 (no delay info)
counter_DW01_inc_0/A17 (no delay info)
```

Connected
gatepins

- ▶ Tracing Gatepin
counter/count_reg[7]/q connections?
- ▶ Tracing Gatepin
counter/count_reg[7]/d connections?

Gatepin-based Connectivity

Gatepins:

 

```

Gate Pin: counter_dw01_inc_0/A17
Connections: (4)
counter_dw01_inc_0/U2/b (no delay info)
counter/count7 (no delay info)
counter/add_13/A17 (no delay info)
counter/\count_reg[7]/q (no delay info)
-----
Gate Pin: counter_dw01_inc_0/SUM17
Connections: (3)
counter_dw01_inc_0/U2/x (no delay info)
counter/add_13/SUM17 (no delay info)
counter/\count_reg[7]/d (no delay info)
-----
Gate Pin: counter/\count_reg[7]/d
Connections: (2)
counter/add_13/SUM17 (no delay info)
counter_dw01_inc_0/SUM17 (no delay info)
-----
Gate Pin: counter/count7
Connections: (3)
counter/add_13/A17 (no delay info)
counter_dw01_inc_0/A17 (no delay info)
counter/\count_reg[7]/q (no delay info)
-----
Gate Pin: counter_dw01_inc_0/U1_1_6/c0
Connections: (1)
counter_dw01_inc_0/U2/a (no delay info)
-----
Gate Pin: counter/\count_reg[7]/q
Connections: (3)
counter/count7 (no delay info)
counter/add_13/A17 (no delay info)
counter_dw01_inc_0/A17 (no delay info)


```

Connected Gatepins

- ▶ Tracing Gatepin
counter/count_reg[7]/q connections?
- ▶ Tracing Gatepin
counter/count_reg[7]/d connections?

Gatepin-based Connectivity

Gatepins: **Next level**

 

```

Gate Pin: counter_DW01_inc_0/A17
Connections: (4)
counter_DW01_inc_0/U2/b (no delay info)
counter/count7 (no delay info)
counter/add_13/A17 (no delay info)
counter/\count_reg[7]/q (no delay info)
-----
Gate Pin: counter_DW01_inc_0/SUM17
Connections: (3)
counter_DW01_inc_0/U2/x (no delay info)
counter/add_13/SUM17 (no delay info)
counter/\count_reg[7]/d (no delay info)
-----
Gate Pin: counter/\count_reg[7]/d
Connections: (2)
counter/add_13/SUM17 (no delay info)
counter_DW01_inc_0/SUM17 (no delay info)
-----
Gate Pin: counter/count7
Connections: (3)
counter/add_13/A17 (no delay info)
counter_DW01_inc_0/A17 (no delay info)
counter/\count_reg[7]/q (no delay info)
-----
Gate Pin: counter_DW01_inc_0/U1_1_6/c0
Connections: (1)
counter_DW01_inc_0/U2/a (no delay info)
-----
Gate Pin: counter/\count_reg[7]/q
Connections: (3)
counter/count7 (no delay info)
counter/add_13/A17 (no delay info)
counter_DW01_inc_0/A17 (no delay info)
    
```

- ▶ Tracing Gatepin
counter/count_reg[7]/q connections?
- ▶ Tracing Gatepin
counter/count_reg[7]/d connections?

Net-based Connectivity Representation

▶ Net

- ▶ A net is a list of gatepins
- ▶ A net may also be a gatepin itself
 - ▶ When it is a module I/O
- ▶ Module I/O gatepin nets are updated
 - ▶ When new modules, new wires and instances are declared

▶ Gatepin

- ▶ Each Gatepin is related to a single Net
- ▶ the associated Net may itself be a gatepin - Module I/O port gatepin
- ▶ The list of gatepins in its net
 - ▶ Are connected gatepins at this level of the hierarchy
 - ▶ The connected gatepins may also be themselves be nets
 - As they may be Module I/O pins down of up in the hierarchy

Net-based Connectivity Representation

- ▶ Net updating
 - ▶ In net-based connectivity gatepin nets must be replaced when a new level of hierarchy is introduced:

Net Replacements for Example

```
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/SUM16 (was counter_DW01_inc_0/SUM16) with counter/internal16
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/SUM17 (was counter_DW01_inc_0/SUM17) with counter/internal17
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/SUM14 (was counter_DW01_inc_0/SUM14) with counter/internal14
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/SUM15 (was counter_DW01_inc_0/SUM15) with counter/internal15
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/SUM12 (was counter_DW01_inc_0/SUM12) with counter/internal12
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/SUM13 (was counter_DW01_inc_0/SUM13) with counter/internal13
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/SUM10 (was counter_DW01_inc_0/SUM10) with counter/internal10
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/SUM11 (was counter_DW01_inc_0/SUM11) with counter/internal11
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/A12 (was counter_DW01_inc_0/A12) with counter/count12
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/A13 (was counter_DW01_inc_0/A13) with counter/count13
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/A10 (was counter_DW01_inc_0/A10) with counter/count10
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/A11 (was counter_DW01_inc_0/A11) with counter/count11
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/A16 (was counter_DW01_inc_0/A16) with counter/count16
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/A17 (was counter_DW01_inc_0/A17) with counter/count17
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/A14 (was counter_DW01_inc_0/A14) with counter/count14
DEBUG: Replacing Original Net of Gatepin counter_DW01_inc_0/A15 (was counter_DW01_inc_0/A15) with counter/count15
```

Net-based Connectivity Representation

► Net updating

- In net-based connectivity gatepin nets must be replaced when a new level of hierarchy is introduced:

Gatepin
counter_DW01_inc_0/SUM|7
before net replacement:

```
-----  
Gate Pin: counter_DW01_inc_0/SUM|7  
Connections: (0)  
(Module counter_DW01_inc_0)  
NONE.  
Net Connection: counter_DW01_inc_0/SUM|7  
(Net) Connections (1):  
counter_DW01_inc_0/U2/x  
-----
```


Gatepin
counter_DW01_inc_0/SUM|7
after net replacement:

```
-----  
Gate Pin: counter_DW01_inc_0/SUM|7  
Connections: (0)  
(Module counter_DW01_inc_0)  
NONE.  
Net Connection: counter/internal|7  
(Net) Connections (3):  
counter/sdd_13/SUM|7  
counter_DW01_inc_0/SUM|7  
counter/\count_reg[7]/d  
-----
```

- Net itself is not modified:


```
-----  
Net Name: counter_DW01_inc_0/SUM|7  
Connections (1):  
counter_DW01_inc_0/U2/x  
-----
```

Partial Schematic

 

Net-based Connectivity

Nets:

 


```
Net Name: counter_DW01_inc_0/A17
Connections (1):
counter_DW01_inc_0/U2/b
-----
Net Name: counter_DW01_inc_0/SUM17
Connections (1):
counter_DW01_inc_0/U2/x
-----
Net Name: counter/internal7
Connections (3):
counter/add_13/SUM17
counter_DW01_inc_0/SUM17
counter/\count_reg[7]/d
-----
Net Name: counter/count17
Connections (3):
counter/add_13/A17
counter_DW01_inc_0/A17
counter/\count_reg[7]/q
-----
Net Name: counter_DW01_inc_0/carry17
Connections (2):
counter_DW01_inc_0/U1_6/co
counter_DW01_inc_0/U2/a
```

- ▶ Tracing Gatepin counter/count_reg[7]/q connections?
 - ▶ Net connection → count[7]
- ▶ Tracing Gatepin counter/count_reg[7]/d connections?
 - ▶ Net connection → internal[7]

Net-based Connectivity

Nets:

 

```

Net Name: counter_DW01_inc_0/A|7
Connections (1):
counter_DW01_inc_0/U2/b
-----
Net Name: counter_DW01_inc_0/SUM|7
Connections (1):
counter_DW01_inc_0/U2/x
-----
Net Name: counter/internal|7
Connections (3):
counter/add_13/SUM|7
counter_DW01_inc_0/SUM|7
counter/count_reg[7]/d
-----
Net Name: counter/count|7
Connections (3):
counter/add_13/A|7
counter_DW01_inc_0/A|7
counter/count_reg[7]/q
-----
Net Name: counter_DW01_inc_0/carry|7
Connections (2):
counter_DW01_inc_0/U1_6/co
counter_DW01_inc_0/U2/a
  
```

- ▶ Tracing Gatepin counter/count_reg[7]/q connections?
 - ▶ Net connection → count[7]
- ▶ Tracing Gatepin counter/count_reg[7]/d connections?
 - ▶ Net connection → internal[7]

▶ 16


CE439 - CAD Algorithms II 28/7/2017

counter_DW01_inc_0/A|7 is of the form
 <modulename>/<portname> is a **direct module port** - also called non-bridging

counter/add_13/SUM|7 is of the form
 <newmodule/instance1/instance2/.../portname> is a bridging gatepin

Bridging gatepins will always possess a direct module port

Net-based Connectivity

 

Nets:

```

Net Name: counter_DW01_inc_0/A|7
Connections (1):
counter_DW01_inc_0/U2/b
-----
Net Name: counter_DW01_inc_0/SUM|7
Connections (1):
counter_DW01_inc_0/U2/x
-----
Net Name: counter/internal|7
Connections (3):
counter/add_13/SUM|7
counter_DW01_inc_0/SUM|7
counter/count_reg[7]/d
-----
Net Name: counter/count|7
Connections (3):
counter/add_13/A|7
counter_DW01_inc_0/A|7
counter/count_reg[7]/q
-----
Net Name: counter_DW01_inc_0/carry|7
Connections (2):
counter_DW01_inc_0/U1_6/co
counter_DW01_inc_0/U2/a
    
```

Gatepin
is also a
Net

Net
gatepins


- ▶ Tracing Gatepin counter/count_reg[7]/q connections?
 - ▶ Net connection → count[7]
- ▶ Tracing Gatepin counter/count_reg[7]/d connections?
 - ▶ Net connection → internal[7]

▶ 17

CE439 - CAD Algorithms II 28/7/2017

counter_DW01_inc_0/A|7 is of the form
 <modulename>/<portname> is a **direct module port** - also
 called non-bridging
 counter/add_13/SUM|7 is of the form
 <newmodule/instance1/instance2/.../portname> is a bridging
 gatepin
 Bridging gatepins will always possess a direct module
 port

Net-based Connectivity

 

Nets:

```

Net Name: counter_DW01_inc_0/A|7
Connections (1):
counter_DW01_inc_0/U2/b
-----
Net Name: counter_DW01_inc_0/SUM|7
Connections (1):
counter_DW01_inc_0/U2/x
-----
Net Name: counter/internal|7
Connections (3):
counter/add_13/SUM|7
counter_DW01_inc_0/SUM|7
counter/count_reg[7]/d
-----
Net Name: counter/count|7
Connections (3):
counter/add_13/A|7
counter_DW01_inc_0/A|7
counter/count_reg[7]/q
-----
Net Name: counter_DW01_inc_0/carry|7
Connections (2):
counter_DW01_inc_0/U1_1_6/co
counter_DW01_inc_0/U2/a
    
```

Gatepin
is also a
Net

Net
gatepins

- ▶ Tracing Gatepin counter/count_reg[7]/q connections?
 - ▶ Net connection → count[7]
- ▶ Tracing Gatepin counter/count_reg[7]/d connections?
 - ▶ Net connection → internal[7]


▶ 18

CE439 - CAD Algorithms II 28/7/2017

counter_DW01_inc_0/A|7 is of the form
 <modulename>/<portname> is a **direct module port** - also
 called **non-bridging**
 counter/add_13/SUM|7 is of the form
 <newmodule/instance1/instance2/.../portname> is a bridging
 gatepin
 Bridging gatepins will always possess a direct module
 port

Net-based Connectivity

Nets:

 

```


Net Name: counter_dw01_inc_0/A17
Connections (1):
counter_dw01_inc_0/U2/b
-----
Net Name: counter_dw01_inc_0/SUM17
Connections (1):
counter_dw01_inc_0/U2/x
-----
Net Name: counter/internal7
Connections (3):
counter/add_13/SUM17
counter_dw01_inc_0/SUM17
counter/count_reg[7]/d
-----
Net Name: counter/count17
Connections (3):
counter/add_13/A17
counter_dw01_inc_0/A17
counter/count_reg[7]/q
-----
Net Name: counter_dw01_inc_0/carry17
Connections (2):
counter_dw01_inc_0/U1_6/co
counter_dw01_inc_0/U2/a
    
```

Net gatepins

- ▶ Tracing Gatepin counter/count_reg[7]/q connections?
 - ▶ Net connection → count[7]
- ▶ Tracing Gatepin counter/count_reg[7]/d connections?
 - ▶ Net connection → internal[7]

Net-based Connectivity

Nets:

 

```

Net Name: counter_dw01_inc_0/A17
Connections (1):
counter_dw01_inc_0/U2/b

Net Name: counter_dw01_inc_0/SUM17
Connections (1):
counter_dw01_inc_0/U2/x

Net Name: counter/internal17
Connections (3):
counter/add_13/SUM17
counter_dw01_inc_0/SUM17
counter/count_reg[7]/d

Net Name: counter/count17
Connections (3):
counter/add_13/A17
counter_dw01_inc_0/A17
counter/count_reg[7]/q


Net Name: counter_dw01_inc_0/carry17
Connections (2):
counter_dw01_inc_0/U1_6/co
counter_dw01_inc_0/U2/a
    
```

Gatepin
is also a
Net
Net
gatepins

- ▶ Tracing Gatepin counter/count_reg[7]/q connections?
 - ▶ Net connection → count[7]
- ▶ Tracing Gatepin counter/count_reg[7]/d connections?
 - ▶ Net connection → internal[7]

Net-based Connectivity

Nets:

 

```

Net Name: counter_DW01_inc_0/A17
Connections (1):
counter_DW01_inc_0/U2/b
-----
Net Name: counter_DW01_inc_0/SUM17
Connections (1):
counter_DW01_inc_0/U2/x
-----
Net Name: counter/internal7
Connections (3):
counter/add_13/SUM17
counter_DW01_inc_0/SUM17
counter/count_req[7]/d
-----
Net Name: counter/count17
Connections (3):
counter/add_13/A17
counter_DW01_inc_0/A17
counter/count_req[7]/q
-----
Net Name: counter_DW01_inc_0/carry17
Connections (2):
counter_DW01_inc_0/U1_6/co
counter_DW01_inc_0/U2/a
    
```

Net gatepins
 Net is also gatepin

- ▶ Tracing Gatepin counter_DW01_inc_0/U2/x connections?
 - ▶ Net connection → counter_DW01_inc_0/SUM17
 - ▶ Net is also a gatepin, must be added and its net traced